


7/7/23

CHAPTER - 3

CURRENT ELECTRICITY

The branch of Physics which deals with the study of electric charges in motion is called Current Electricity.

★ CHARGE CARRIERS

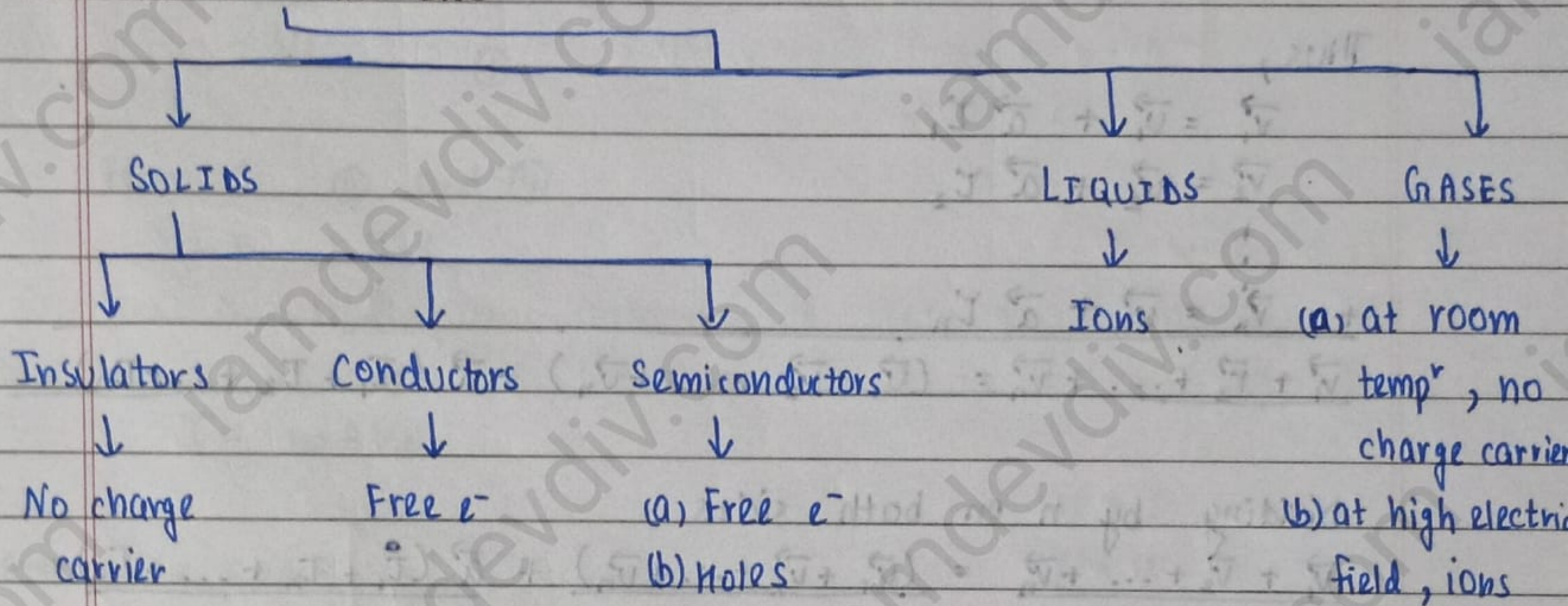

★ DRIFT VELOCITY

The average velocity acquired by free e^- of a conductor under the influence of ^{external} electric field applied is called drift velocity.

10^{28} free e^- / volume

No field $\Rightarrow 10^5$ m/s

External field $\Rightarrow 10^{-4}$ m/s

• EXPRESSION OF DRIFT VELOCITY

If $\vec{u}_1, \vec{u}_2, \dots, \vec{u}_n \Rightarrow$ Initial thermal velocity of free e^-

$$\vec{u}_{avg} = \frac{\vec{u}_1 + \vec{u}_2 + \dots + \vec{u}_n}{n} = 0$$

The force experienced by a free e^- due to external field

$$\vec{F} = -e\vec{E} \quad \text{--- (1)}$$

$$\vec{F} = ma \quad \text{--- (2)}$$

From (1) and (2),

$$m\vec{a} = -e\vec{E}$$

$$\Rightarrow \vec{a} = \frac{-e\vec{E}}{m} \quad \text{--- (3)}$$

Thus,

$$\vec{v}_1 = \vec{u}_1 + \vec{a} \tau_1$$

$$\vec{v}_2 = \vec{u}_2 + \vec{a} \tau_2$$

⋮

$$+ \vec{v}_n = \vec{u}_n + \vec{a} \tau_n$$

$$\vec{v}_1 + \vec{v}_2 + \dots + \vec{v}_n = (\vec{u}_1 + \vec{u}_2 + \dots + \vec{u}_n) + \vec{a} (\tau_1 + \tau_2 + \dots + \tau_n)$$

Dividing by n on both sides

$$\frac{\vec{v}_1 + \vec{v}_2 + \dots + \vec{v}_n}{n} = \frac{(\vec{u}_1 + \vec{u}_2 + \dots + \vec{u}_n)}{n} + \vec{a} \underbrace{(\tau_1 + \tau_2 + \dots + \tau_n)}_n$$

τ_{avg} (Average Relaxation time)

$$\vec{v}_d = \vec{a} \tau_{avg} \quad \text{--- (4)}$$

From (3) and (4),

$$\vec{v}_d = \frac{-eE\tau_{avg}}{m}$$

In magnitude,

$$v_d = \frac{eE\tau_{avg}}{m}$$

• RELATION BETWEEN I AND V_d


$$I = \frac{q}{t} \quad \text{--- (1)}$$

Let $n \Rightarrow$ number density (no. of free e^- / unit volume)

$N \Rightarrow$ Total no. of free e^-

$$N = nAl \quad \text{--- (2)}$$

$$Q = Ne = nAle \quad \text{--- (3)}$$

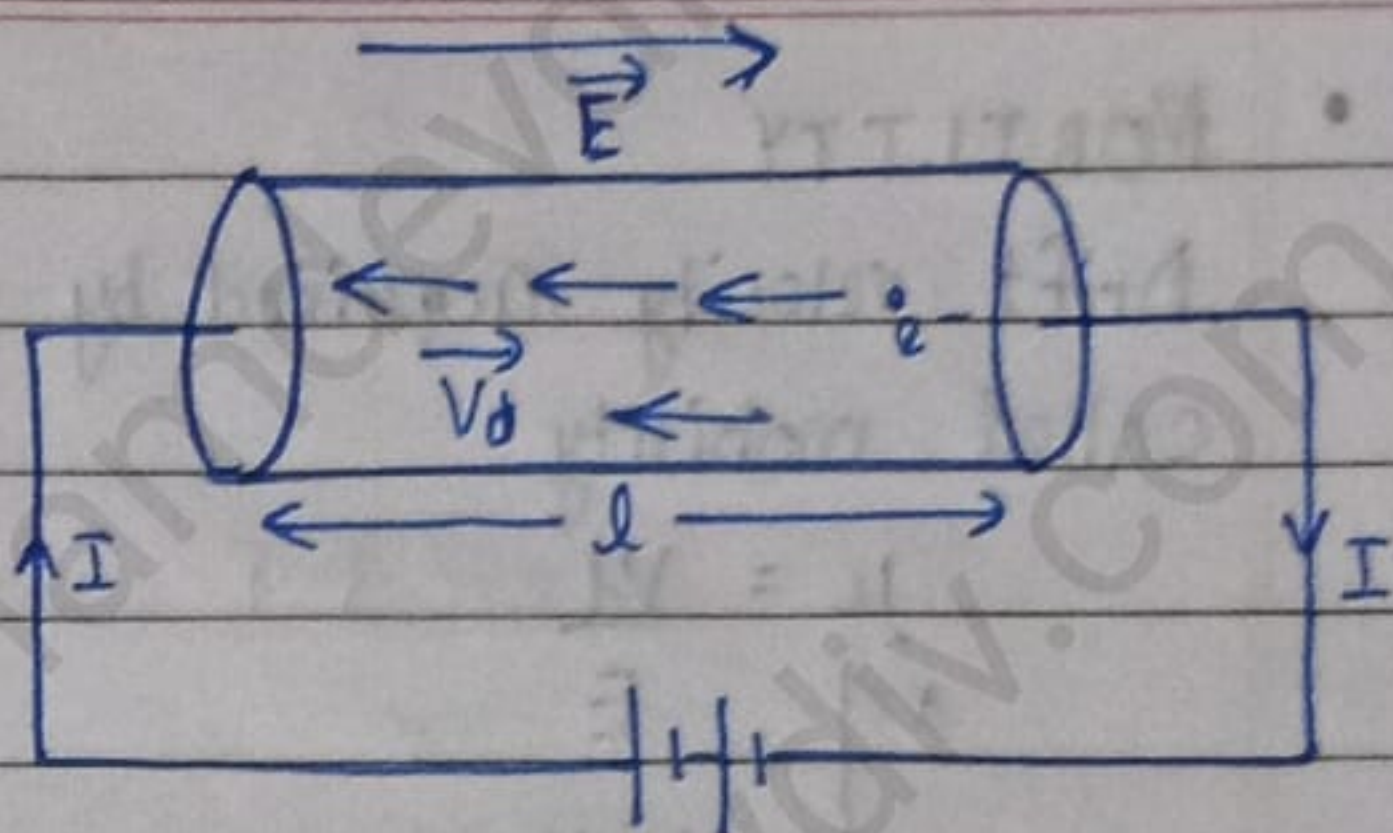

If $l =$ length of conductor,

$$t = \frac{l}{V_d} \quad \text{--- (4)}$$

From (1), (3) and (4)

$$I = \frac{nAle}{t}$$

$$I = \frac{nAle}{\frac{l}{V_d}}$$

$$I = neAV_d$$

NOTE \rightarrow

$$I = neAV_d$$

$$\downarrow \quad \rightarrow \quad \frac{eEt}{m}$$

$$\Rightarrow I = \frac{ne^2AEt}{m}$$

• CURRENT DENSITY

The current flowing per unit area of a conductor is called current density.

$$J = \frac{I}{A}$$

$$\text{OR } \vec{J} = \frac{\vec{I}}{A}$$

$$I = \vec{J} \cdot \vec{A} = J A \cos \theta$$

~~Unit~~

Unit $\Rightarrow A/m^2$

Dimensional Formula $\Rightarrow [AL^{-2}]$

Nature \Rightarrow Vector

• MOBILITY

Drift velocity acquired by a free e^- per unit applied electric field is called mobility.

$$\mu = \frac{V_d}{E}$$

a

$$(a) \text{Unit} \Rightarrow \frac{\text{m/s}}{\text{N/c}} = \text{m A/N}$$

$$(b) \text{Unit} \Rightarrow \frac{\text{m/s}}{\text{V/m}} \Rightarrow \text{m}^2/\text{V-s}$$

★ Ohm's LAW

At constant temperature, the current flowing through a conductor is directly proportional to the potential difference across its ends.

$$I \propto V$$


$$V \propto I$$

$$V = IR$$

Here, $R = \frac{V}{I}$ = Resistance of conductor

$$I$$
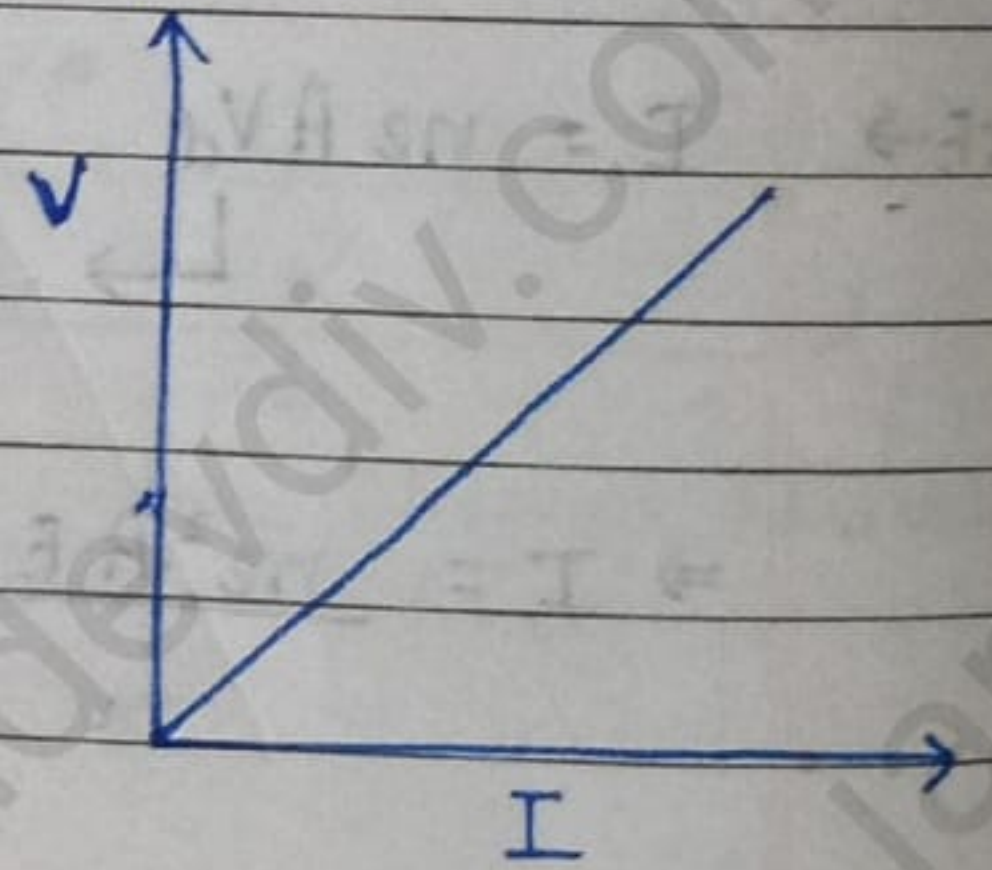
$$\rightarrow \text{Unit} = \text{ohm } (\Omega)$$



• PROOF

$$I = neAV_d \quad \text{--- (1)}$$

$$V_d = \frac{eE\tau}{m} \quad \text{--- (2)}$$

$$E = \frac{V}{l} \quad \text{--- (3)}$$

We get,

$$I = \frac{ne^2 A E \tau}{m}$$

$$I = \frac{ne^2 A V T}{mL}$$

$$\frac{V}{I} = \frac{mL}{ne^2 T A} \rightarrow \text{constant}$$

$$R = \frac{mL}{ne^2 T A}$$

$$R = \frac{mL}{ne^2 T A}$$

• CONDUCTANCE

The reciprocal of resistance is called conductance.

$$G = \frac{1}{R}$$

Unit \Rightarrow (a) $\text{ohm}^{-1} (\Omega^{-1})$
 (b) mho (Ω)
 (c) Siemens (S)

• RESISTIVITY

$$\rho = \frac{RA}{l} = \frac{m}{ne^2 T}$$

Unit \Rightarrow ohm-m ($\Omega\text{-m}$)

• CONDUCTIVITY

$$\sigma = \frac{1}{\rho}$$

Unit ρ
 (a) $(\text{ohm-m})^{-1} (\Omega\text{-m})^{-1}$
 (b) $\text{mho-m}^{-1} (\Omega\text{-m})^{-1}$
 (c) Siemens-m⁻¹ (S-m⁻¹)

• VECTOR FORM (μ -SCOPIC FORM) OF OHM'S LAW

$$I = neA V_d \quad \text{--- (1)}$$

$$V_d = \frac{eE T}{m} \quad \text{--- (2)}$$

From (1) and (2)

$$I = \frac{ne^2 A E \tau}{m}$$

$$\frac{I}{A} = \frac{ne^2 E \tau}{m}$$

$$\therefore \frac{I}{A} = J$$

$$J = \frac{ne^2 E \tau}{m} = \frac{E}{\frac{m}{ne^2 \tau}} \quad \therefore \frac{m}{ne^2 \tau} = \rho$$

$$J = \frac{1}{\rho} E$$

ρ

$$J = \sigma E$$

$$\therefore \vec{J} = \sigma \vec{E}$$


★ KIRCHHOFF'S ~~CONSTANT~~ CURRENT LAW (KCL) OR JUNCTION RULE

According to KCL, the algebraic sum of all currents entering or leaving at a junction is zero.

$$\sum I = 0$$

$$I_1 - I_2 + I_3 - I_4 + I_5 = 0$$

$$I_1 + I_3 + I_5 = I_2 + I_4$$

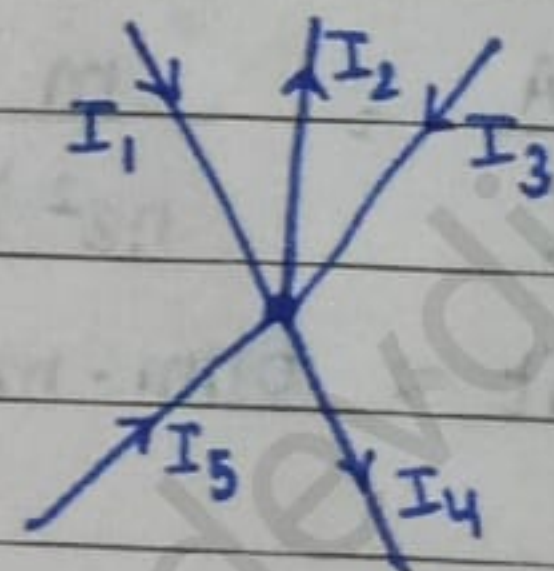

$$\sum I_{in} = \sum I_{out}$$

NOTE → KCL is based on the principle of conservation of charge

★ KIRCHHOFF'S VOLTAGE LAW (KVL) OR LOOP RULE


According to KVL, the algebraic sum of all potentials in a closed network is zero.

$$\sum V = 0$$

OR

$$\sum IR = 0$$

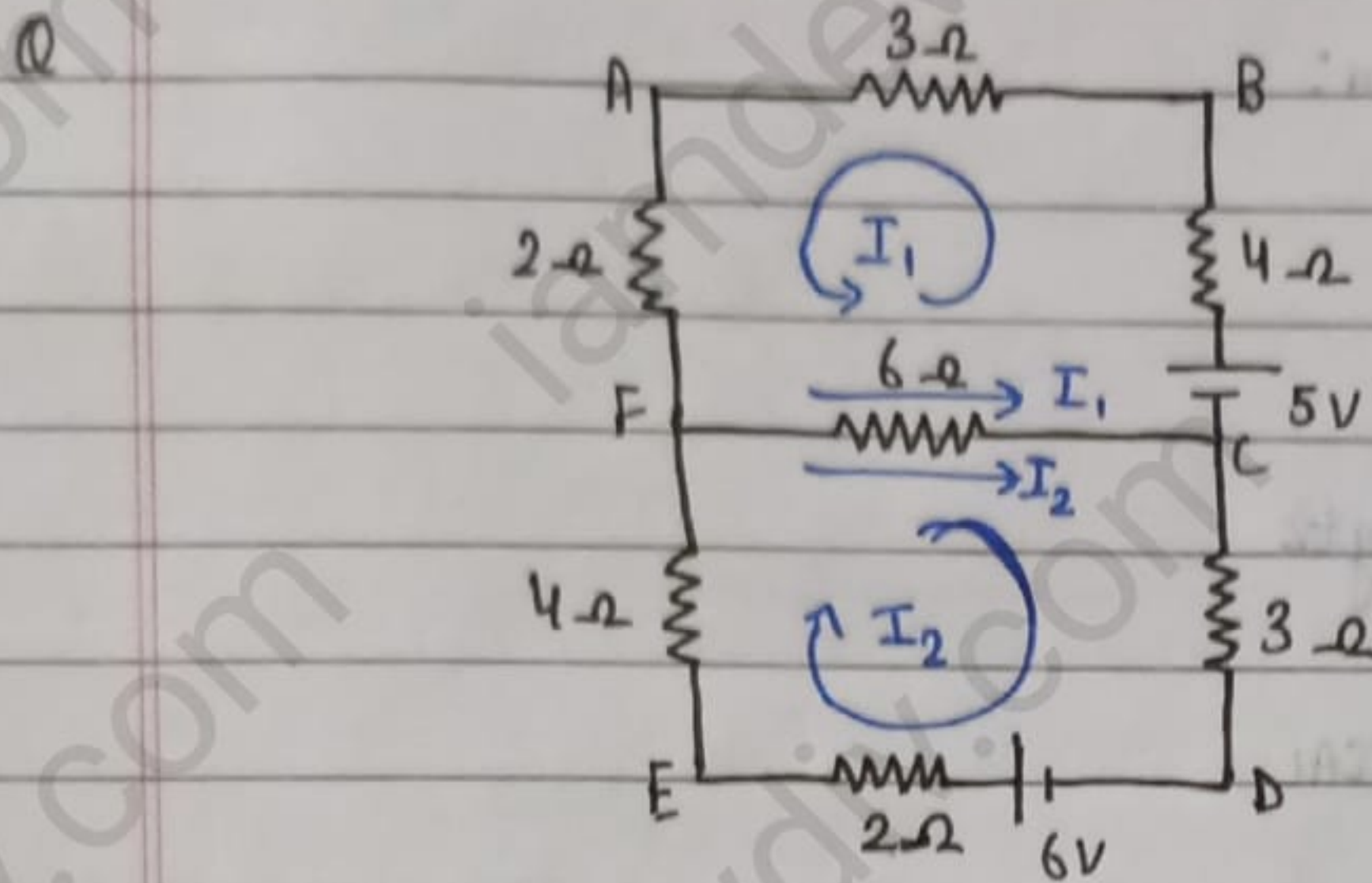NOTE → KVL is based on principle of conservation of energy.



Find $I_{6\Omega}$.

Sol. Applying KVL in loop-1 (AFBA)

$$2I_1 + 6(I_1 + I_2) - 5 + 4I_1 + 3I_1 = 0$$

$$15I_1 + 6I_2 = 5 \quad \text{--- (1)}$$

Applying KVL in loop-2 (FCDEF)

$$6(I_1 + I_2) + 3I_2 - 6 + 2I_2 + 4I_2 = 0$$


$$6I_1 + 15I_2 = 6 \quad \text{--- (2)}$$

Solving (1) and (2),

$$I_1 = \frac{13}{63} \text{ A}, \quad I_2 = \frac{20}{63} \text{ A}$$

$$I_{6\Omega} = I_1 + I_2 = \frac{13}{63} + \frac{20}{63} = \frac{33}{63} = \frac{11}{21} \text{ A} \quad \underline{\underline{\text{Ans}}}$$

★ EMF (ELECTROMOTIVE FORCE)

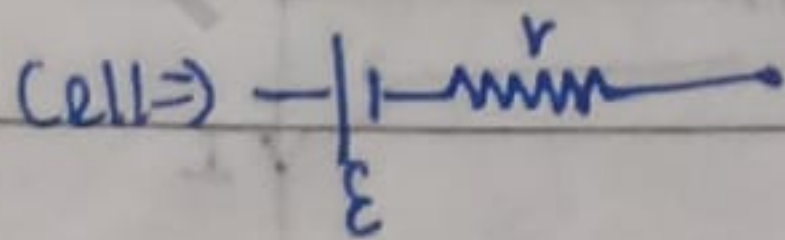

Used to maintain constant voltage.

Consists of - electrolyte (electrolysis)

Low for new cell (2-5 ohms)

Internal resistance depends upon:

- (i) Nature of electrodes
- (ii) Concentration of electrolyte
- (iii) Separation between electrode
- (iv) Level of electrodes in electrolyte

• EMF V/S TERMINAL POTENTIAL

(a) EMF of a cell is potential difference across the terminal of cell/battery when it is not connected with battery. (Unit - Volt)

(OR)

Amount of work done in moving unit charge from low potential to higher potential.

(b) Terminal potential is the potential difference when connected to cell.

NOTE → EMF > Terminal potential

When external force is applied ⇒ EMF < Terminal potential

• RELATION BETWEEN EMF AND INTERNAL RESISTANCE OF A CELL

EMF = Potential drop across internal resistance (r)


+ Potential drop across load resistance

$$E = Ir + IR$$

$$\therefore V = IR$$

$$\Rightarrow E = V + Ir$$

$$\hookrightarrow E > V$$

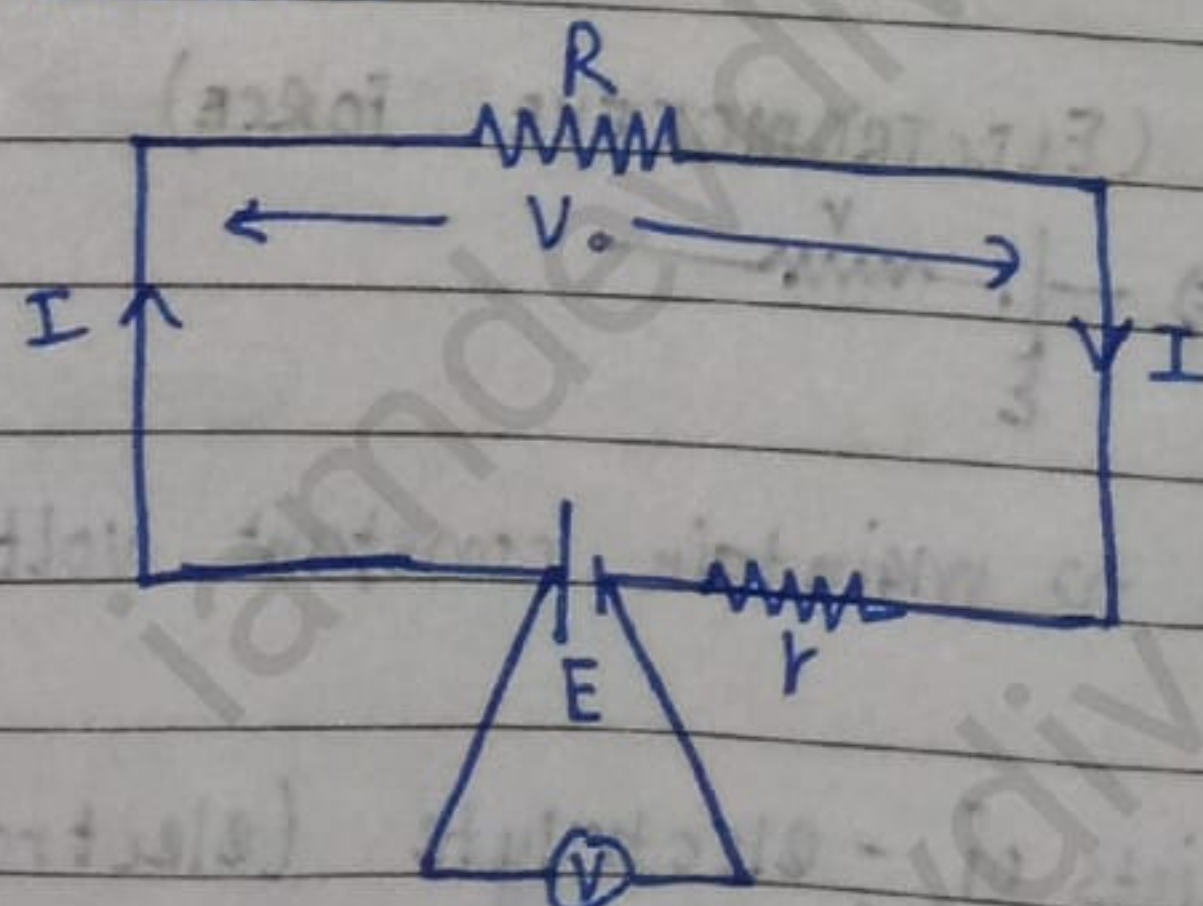


In case of charging,

$$E = V - Ir$$

$$\Rightarrow E < V$$

★ WHEATSTONE BRIDGE

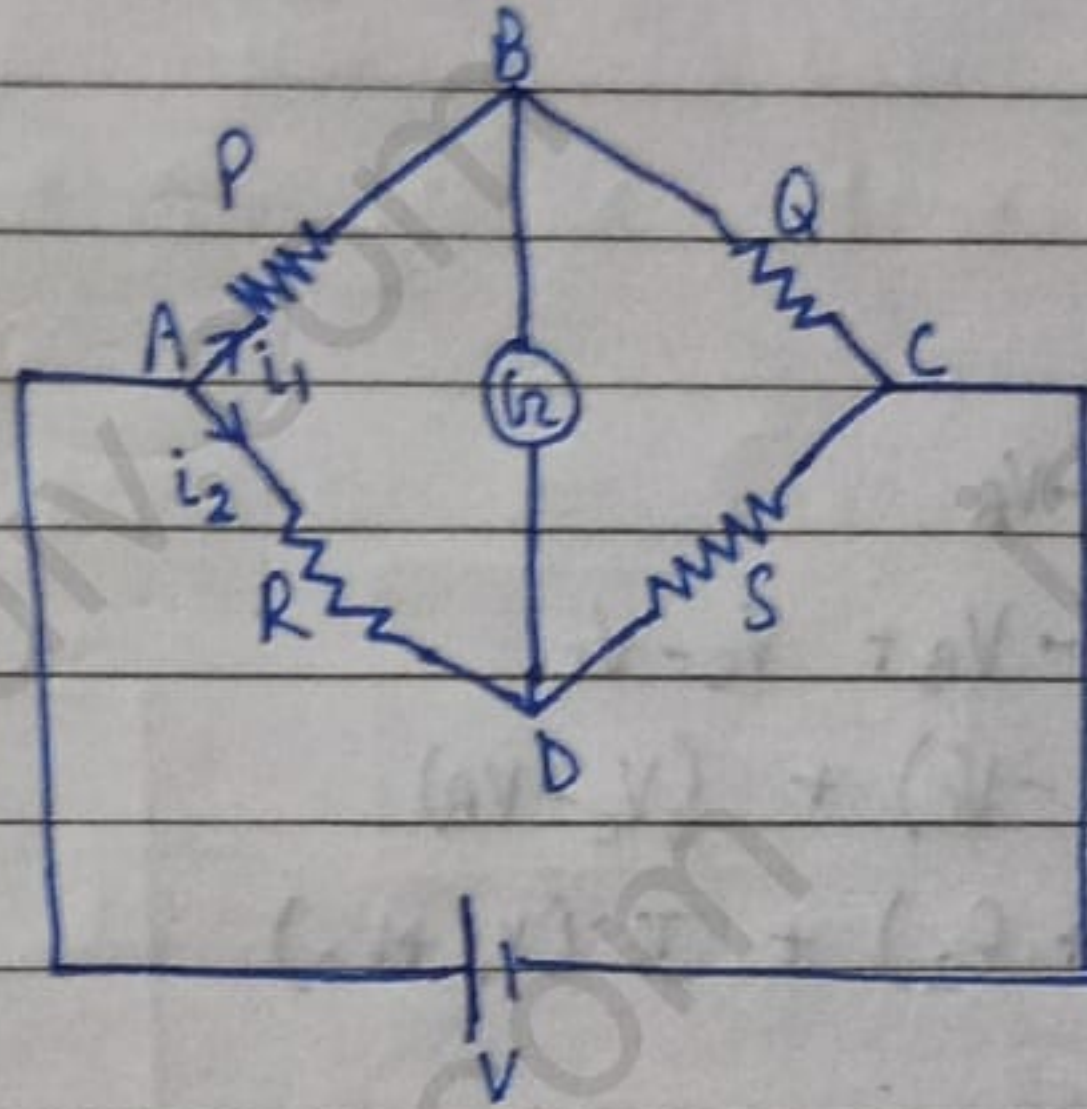

In loop ABDA,

$$\sum V = 0$$

$$\Rightarrow i_1 P - i_2 R = 0$$

$$\Rightarrow i_1 P = i_2 R \quad \text{--- (1)}$$

In loop BCDB,

$$\sum V = 0$$

$$\Rightarrow i_2 S - i_1 Q = 0$$

$$\Rightarrow i_1 Q = i_2 S \quad \text{--- (2)}$$


$$\text{(1)} \div \text{(2)},$$

$$\frac{i_1 P}{i_1 Q} = \frac{i_2 R}{i_2 S}$$

$$\Rightarrow \frac{P}{Q} = \frac{R}{S}$$

★ GROUPING OF TWO UNIDENTICAL CELLS

• SERIES GROUPING

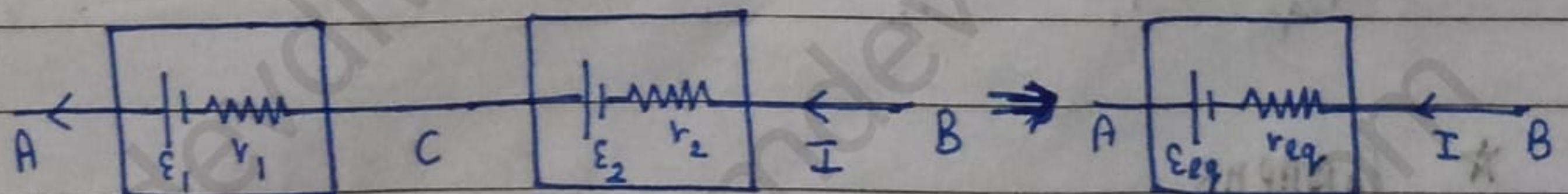

For cell 1,

$$V_{AC} = V_A - V_C$$

$$= \mathcal{E}_1 - Ir_1 \quad \text{--- (1)}$$

For cell 2,

$$\begin{aligned} V_{CB} &= V_C - V_B \\ &= \mathcal{E}_2 - Ir_2 \end{aligned}$$

For equivalent cell,


$$\begin{aligned} V_{AB} &= V_A - V_B \\ \mathcal{E}_{eq} - I r_{eq} &= V_A - V_B \\ &= V_A - V_B + V_C - V_C \\ &= (V_A - V_C) + (V_C - V_B) \end{aligned}$$

$$\mathcal{E}_{eq} - I r_{eq} = (\mathcal{E}_1 + \mathcal{E}_2) + I (r_1 + r_2)$$

$$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2$$

$$r_{eq} = r_1 + r_2$$

• PARALLEL COMBINATION

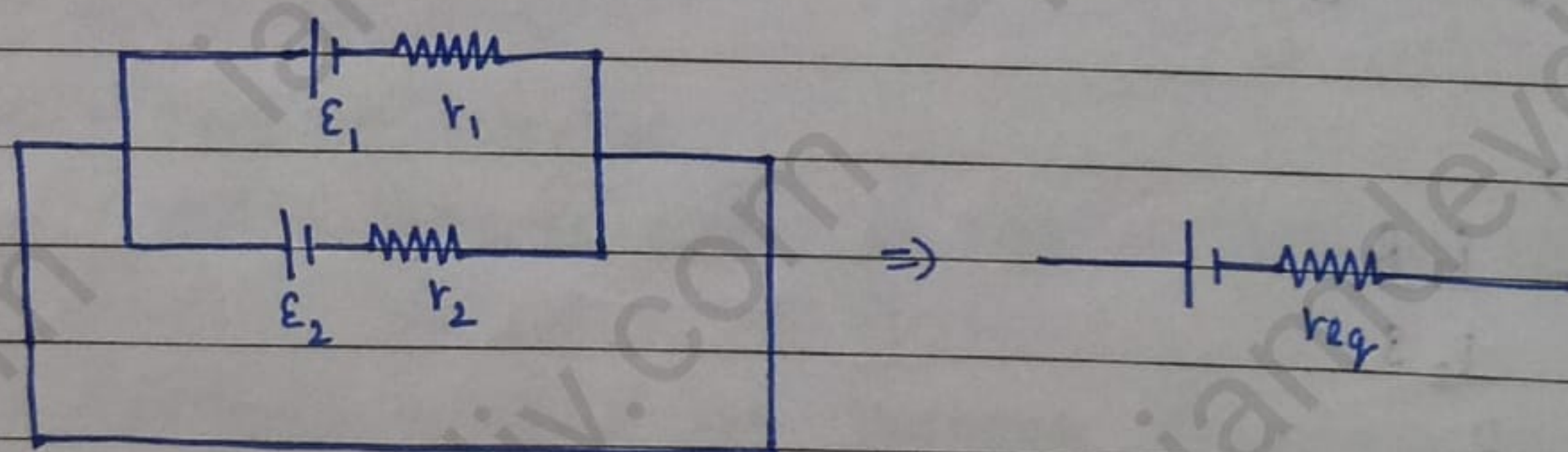


Net EMF $\Rightarrow E$ (parallel combination, V is same)

$$r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$


$$\Rightarrow \frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2}$$

★ GRAPHS

• EMF v/s R

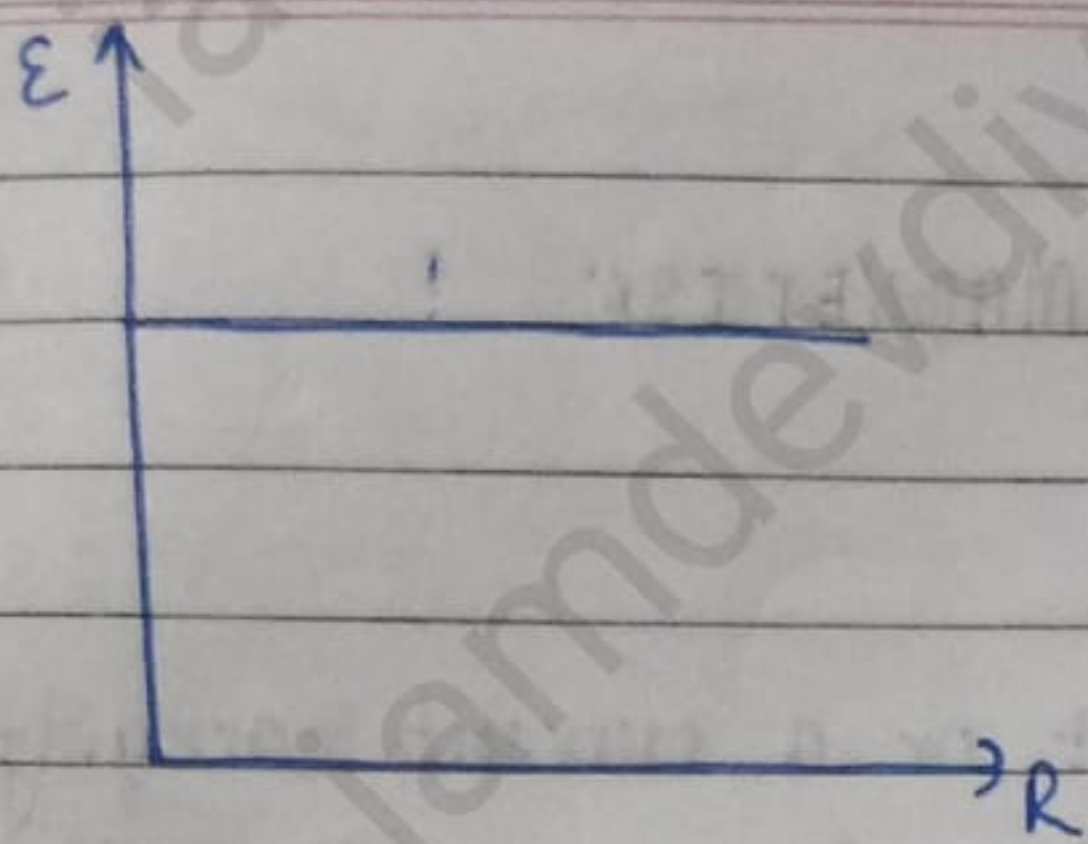

• V vs R

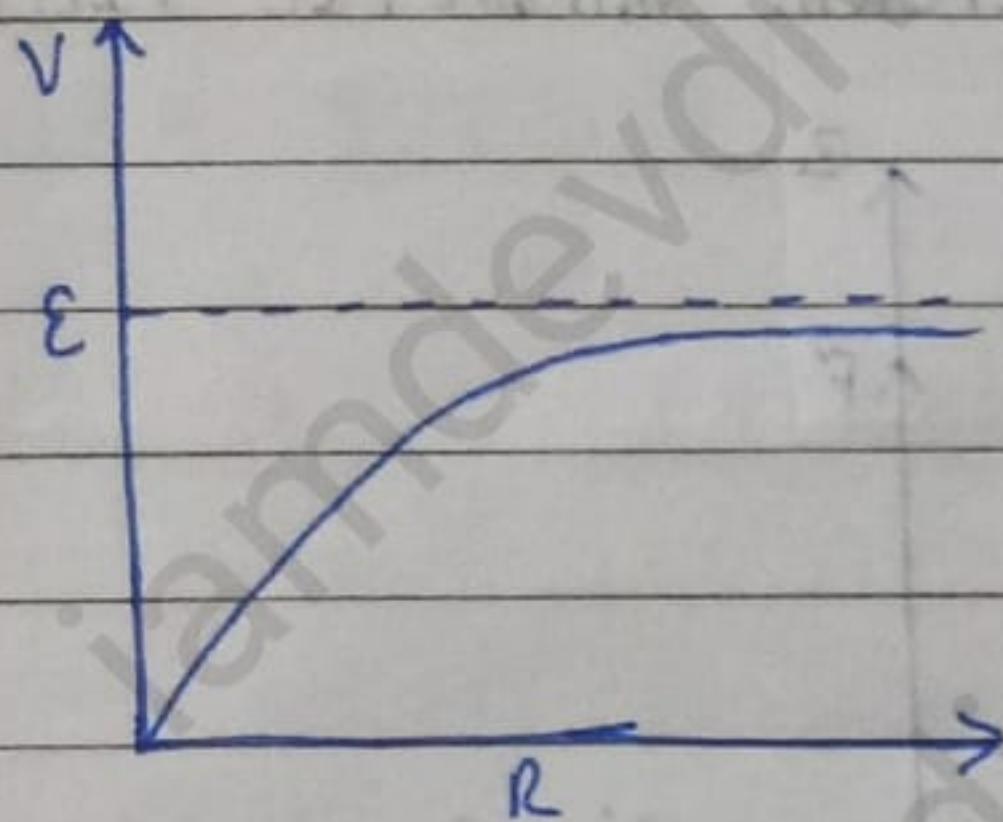

• V vs I

